# Pipeline MIPS Architecture

# Assumptions

- 1. Setting Reset signal on high will reset PC (=0).
- 2. Instruction Memory has 16 Memory Locations each memory location is 32-bit wide.
- 3. Data Memory has 16 Memory Locations each memory location is 32-bit wide.
- 4. Whenever the Program Counter is out of bound i.e. greater than 16. NOP is executed, to go back to initial state Reset should be made ON.

## Instructions Implemented

- a. NOP
- b. R-Type: AND, OR, ADD, SUB, SLT, NOR
- c. LW, SW
- d. I-Type: ADDI, ANDI, LUI, ORI, SLTI, d. Branch: BEQ

## Datapath

(diagram has been spilt into three parts for better understanding)

 


Fig.1 Pipelined Datapath

 


Fig.2 Datapath with Forwarding Unit

 


Fig.3 Datapath with Hazard Detection

# Modules and their Functions

- 1. mux\_32x2: A 32bit X 2-input multiplexer with 1-bit control and one output.
- 2. mux\_32x3: A 32-bit X 3-input multiplexer with 2-bit control and one output.

3.	mux_11x2: A 11-bit X 2-input multiplexer with 1-bit control and one output.
4.	mux_5x2: A 5-bit X 2-input multiplexer with 1-bit control one output.
5.	simple_alu_32bit: A simple 32-bit ALU with only one operation i.e. addition. It is used in calculation of next PC. Firstly, to calculate PC+1 and then for PC+1+Offset.
6.	instr_mem: instruction memory which space for 16 32-bit instructions and it can be expanded further very easily. It takes PC as input and provides the instruction corresponding to it.
7.	hazard_detect_unit: A hazard detection unit for generating signals to cope with hazards caused by LW instruction. It takes ID/EX.MemRead, ID/EX.RegisterRt, IF/ID.RegisterRs, and IF/ID.RegisterRt as input and provide output Control for 11 bit MUX used, IF/IDWrite, PCWrite.
8.	compare_hazard: A hazard detection unit for generating signals to cope with hazards caused by BEQ instruction. It takes ReadData1, ReadData2 and Branch as input and provides IF/IDFlush and PCSrc as output.
9.	ctrl_unit: Main control unit to generate signals for 32-bit 2-input multiplexers, 5-bit 2-input multiplexer and main ALU. It takes IF/ID.Opcode as input and provides control signals (aluOp, regDst, aluSrc, memToReg, regWrite, memWrite, memRead, branch)
10.	registers_file: This module is used for 32 32-bit registers with ability to read or change their content.
11.	sign_extend: It sign extends a 16-bit binary number to a 32-bit binary number. Used by LW and SW instruction to generate a 32-bit offset.
12.	forwarding_unit: This module generates control signals, required by forwarding multiplexers, depending on different conditions.

- 13. alu\_ctrl\_unit: This module generates control signals required for main ALU w.r.t inputs (which are ALUOp and Function)
- 14. alu\_32bit: This module is for the main ALU. It can perform add, sub, and, or, nor, less than, equal to.
- 15. data\_mem: This module is the RAM of the system. It can store up to 16 32-bit of data which can be extended further very easily.
- 16. pipeline\_mips\_32bit: This module is the main one. It combines and completes all the connections required by the above modules to work and form a Pipeline MIPS Architecture.
- 17. testbench: this unit is the testbench for pipeline mips 32bit module.

#### Examples

### Initial Content of Register File.

```
0000001d
0000001ь
```

#### Initial Content of Data Memory

0000000f	000000000000000000000000000000000000000	000000000000000000000000000000000000000
D000000d	000000000000000000000000000000000000000	000000000000000000000000000000000000000
	000000000000000000000000000000000000000	
00000009	000000000000000000000000000000000000000	000000000000000000000000000000000000000
	000000000000000000000000000000000000000	
00000005	000000000000000000000000000000000000000	000000000000000000000000000000000000000
	000000000000000000000000000000000000000	
00000001	000000000000000000000000000000000000000	000000000000000000000000000000000000000

1.

#### After implementing the instructions

#### Register File -

### Data Memory -